
```
TSS
     fo=22KHz
                                                                                        fs = 17 KHZ -> (fs)=16dB Ws = 17/22
        9=5
                                                                                      fs2 = 36KHz → x (fs2) = 24db Ws2 = 36/22
      MAX= 0,5dB
           f_1f_2? \rightarrow \omega_1\omega_2 = 1 \wedge Q = \frac{\omega_0}{\omega_2 - \omega_1} \Rightarrow \omega_1\omega_2 = Q(\omega_2 - \omega_1) \rightarrow \omega_1(\omega_2 + Q) = Q\omega_2 \rightarrow \omega_1 = \frac{\omega_2Q}{\omega_2 + Q} \rightarrow 1 = \frac{\omega_2^2Q}{\omega_2 + Q} \rightarrow \omega_2^2Q - \omega_2 - Q = 0
             => W2 = 1+ 1101 = 1,104987562 → W1 = 0,4049875622
           N_s = 9. \frac{\omega_s^2 - 1}{\omega_s} \rightarrow \Omega_{s_1} = -2,606951872 D_{s_2} = 5,126262626
         ξ2= 10 α44×/0-1 = 0,1220184543 → ξ=0,3483114002
        αμίν = 10tag (1+ ξ²cosh² [ncosh-1(sus)]) -> ακ sus; n=3 (α=26,866dB) sus; n=2 (α=25,123dB) => n=3
        Q = \frac{1}{N} \Delta \epsilon_n h^{-1} \left( \frac{1}{\epsilon} \right) = 0.5913783794
        Polos: T_{k} = -senh(a) sen(\frac{2k-1}{2n}\pi)  W_{k} = conh(a) cos(\frac{2k-1}{2n}\pi)  \longrightarrow \begin{cases} -0.3132282432 + j1.021927491 \\ -0.6264564863 \\ -0.3132282432 - j1.021927491 \end{cases}
Uhio Decollectures \pi = \frac{3}{2} + \frac{1}{2} \pi = \frac{1}{2}
                            Wolf= 96264864865 Wo2= 1,14244773
        T(\$) = 0.626 \times \frac{1.142}{\$ + 0.626} \times \frac{1.142}{\$^2 + 0.626} \times \frac{1.142}{\$ + 1.142} = \frac{a}{\$ + a} \cdot \frac{c}{\$^2 + b\$ + c} \leftarrow \text{Transferencia posabojos prototipo}
   Transformación LP-BP Núcleo: Sh(w)= Q w2+1 -> $(5)=Q 52+1
             \hat{b}.z: \frac{\alpha}{\sqrt{s_{s+1}} + \alpha} = \frac{z_s \alpha \sqrt{\alpha}}{z_s + s_s \alpha + 1}
           C.c: \frac{c}{\left(Q(\frac{S^2+1}{S})^2 + b\left(Q(\frac{S^2+1}{S}) + C\right)^2 + \frac{Q^2}{S^2}\left(S^4 + 2S^2 + 1\right) + b \cdot \frac{Q}{S}(S^2 + 1) + C} = \frac{c \cdot S^2/Q^2}{S^4 + S^3(b/Q) + S^2(2 + C/Q^2) + S(b/Q) + 1}
    \Rightarrow T(s) = \frac{s \cdot \alpha/\alpha}{s^2 + s \cdot \frac{\alpha}{\alpha} + 1} \cdot \frac{s^2 \cdot c/\alpha^2}{s^4 + s^3 \left(\frac{b}{\alpha}\right) + s^2 \left(2 + \frac{c}{\alpha^2}\right) + s \left(\frac{b}{\alpha}\right) + 1} \quad \sim \Rightarrow \frac{\alpha}{q} = 0,1252912973 = b \quad \frac{C}{q^2} = 0,0456979092
  Descomposición de un sos:
                 Polon: -0,02813691233± j 0,9025322821 → Wo= 0,902970767 = 16,04601868 → Se cumple ignal & y wo,= wo= 1,107455564 & = 16,04601736
|\text{Primero Sección}| \rightarrow \omega_0 = 1 \quad q = \frac{Q}{a} = 7,981400317
=) T(s) = \frac{S.0,125}{S^2 + S.0,12S + 1} \cdot \frac{S.0,056}{S^2 + S.0,056 + 0,815} \cdot \frac{S.0,069}{S^2 + S.0,069 + 1,226} \cdot \frac{0,046}{0,056.0,059} \quad \text{La transferencia} 
the majority of the prime of 
                                                                                                                                                                                                                                                                                                                                                                raquière de gonomice
        T(s) = \frac{6}{sc + \frac{1}{sL} + 6} = \frac{s G/c}{s^2 + s \frac{6}{c} + \frac{1}{Lc}} = \frac{s G/c}{s^2 + s \frac{6}{c} + \frac{1}{Lc}}
                                                                                                                                                                                                                                                                                                                                                              V_1
V_0 = V_1 \cdot 1 + \frac{R_1}{R_2}
\frac{R_2}{R_2} = 10,76605617 \rightarrow R_2 = 1
\frac{R_2}{R_2} = 10,76605617
                                                                                                 C=1 -> 1/2= Wo2 -> L= 1/wo2 1/R= 6= Wo/q -> R= 9/wo
              SOS1: {R=17,77025267 L=1,226457826 C=1 }
             SOS2: {R=14,4840846 L=0,815356206 C=1}
```

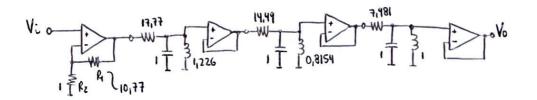

```
fr= 17kHz -> x(fs)=16db -> ws1=17/22
  to= 22KH2
                         fsz=361412 → a (fsz)=24db → wsz=36/22
  9=5
  Sb2,0 = xanp
  fifz? - wiwz=1 ~ Q= wo = wiwz=Q(wz-w) - wikez+Q)=w2 - wi= Quz
  \omega_{1} = \omega_{2} = \omega_{2} \rightarrow \omega_{2} + Q = Q \omega_{2}^{7} \rightarrow \omega_{2}^{2} - \omega_{2} \cdot 1 = 0 \rightarrow \omega_{2} = \frac{1 + \sqrt{101}}{10} = 1,104987562 \rightarrow \omega_{1} = 0,9049875622
 JUSZ= 1,025252525
 ξ²= 1 10 αμαίλο 1 = 0,1220184543 ξ = 0,3493114002
 QHIN = 10 log (1+ €2 cosh = [n cosh - (Ns)]) → Ns1: n=3 (x=26,866 dB) Sls2: n=2 (x=25,123dB)
 a = \frac{1}{n} \cos \theta \sinh^{-1}\left(\frac{1}{\epsilon}\right) = 0.5913783794 \forall k = -\sinh(a) \cdot \sinh\left(\frac{2k-1}{2n}\pi\right) \forall k = \cosh(a) \cdot \cosh\left(\frac{2k-1}{2n}\pi\right)
 Polo : (-0,3132282432+11.021927491} - T($) = 0,626 1,142
-0,6264564863+10
         -0,3132282432 - 11,021927491) W. = 4,026263632 &= 1,706189477 - W. = 0,6264564865
                             T(\$) = \underbrace{a}_{\$+a} \underbrace{c}_{\$^2+b.\$+c} \begin{cases} a = 0,6264564863 \\ b = a \\ c = 1,14244773 \end{cases}
                                  E Transferencia posobojos prototipo.
                            Nucleo de tranf: R(\omega) = \frac{(\omega^2 + \omega) \cdot Q}{(\omega)} \rightarrow \$(s) = \frac{S^2 + 1}{S} \cdot Q
T(s)=
        \frac{Q}{Q \cdot \frac{S^2+1}{S} + Q} \cdot \frac{C}{(Q \cdot \frac{S^2+1}{S})^2 + Q \cdot \frac{S^2+1}{S} \cdot \frac{D}{S} + C} = \frac{S \cdot QQ}{S^2 + \frac{1}{S} \cdot \frac{Q}{Q} + 1}
       \frac{s^{2}/\alpha^{2} \cdot c}{(s^{2}+1)^{2} \cdot \frac{s}{9}(s^{2}+1) \cdot b + \frac{s^{2}c}{9^{2}}} = \frac{s^{2}/\alpha^{2} \cdot c}{(s^{4}+2s^{2}+1) + (s^{3}\cdot b/q + s\cdot b/q) + s^{2}\cdot c/q^{2}} = \frac{s^{2}/\alpha^{2}\cdot c}{s^{4}+s^{3}(b/q)+s^{3}(2+c/q) + s(b/q) + 1}
=> TBP(s)= S.9/Q . S4+S2(b/Q)+S2(2+4Q)+S(b/Q)+1
                                                                           John: -0,0240,3792021+j0,7902938082
                                                                                      90 (1264176778
  a/a=0,1252912973 & Descompenición um sos:
  b/a= >
                               $ = 1,04051735 \ S = 1,714292034 → Hay algo wal.
  4a=0,228489546
  2+6/4=2,228489546
                                 52 C = (5.5c)2 (Coeficiente de la parte cora an los sos) - 10 /4/14/14 k, = 0,2254557897? NO
                        Wb. k= 10 , k= (10/Q) → 00 k= 4,435459392 k2=2,772805319
```

